

ADD_test

```
VSIM 10> run  
# time = 0, A=000000000000000000011111111111111110, B=00000001111111000111000000000001, S=000, Result=000000011111110011011111111111  
# time = 10, A=0000000001111111000000000000000000, B=00000011111111111111000111000001, S=000, Result=00001000111111011111000111000001
```

32 bit adder: hard coded for 32 bit numbers. It does operation bit-by-bit

```

module Adder_32b (S,C,A,B,C0);
input [31:0] A,B;
input C0;
output C;
output [31:0] S;

wire C1,C2,C3,C4,C5,C6,C7,C8,C9,C10,C11,C12,C13,C14,C15,C16,C17,C18,C19,C20,C21,C22,C23,C24,C25,C26,C27,C28,C29,C30,C31;
full_adder FA0(S[0], C1, A[0], B[0], 1'b 0),
FA1(S[1], C2, A[1], B[1], C1),
FA2(S[2], C3, A[2], B[2], C2),
FA3(S[3], C4, A[3], B[3], C3),
FA4(S[4], C5, A[4], B[4], C4),
FA5(S[5], C6, A[5], B[5], C5),
FA6(S[6], C7, A[6], B[6], C6),
FA7(S[7], C8, A[7], B[7], C7),
FA8(S[8], C9, A[8], B[8], C8),
FA9(S[9], C10, A[9], B[9], C9),
FA10(S[10], C11, A[10], B[10], C10),
FA11(S[11], C12, A[11], B[11], C11),
FA12(S[12], C13, A[12], B[12], C12),
FA13(S[13], C14, A[13], B[13], C13),
FA14(S[14], C15, A[14], B[14], C14),
FA15(S[15], C16, A[15], B[15], C15),
FA16(S[16], C17, A[16], B[16], C16),
FA17(S[17], C18, A[17], B[17], C17),
FA18(S[18], C19, A[18], B[18], C18),
FA19(S[19], C20, A[19], B[19], C19),
FA20(S[20], C21, A[20], B[20], C20),
FA21(S[21], C22, A[21], B[21], C21),
FA22(S[22], C23, A[22], B[22], C22),
FA23(S[23], C24, A[23], B[23], C23),
FA24(S[24], C25, A[24], B[24], C24),
FA25(S[25], C26, A[25], B[25], C25),
FA26(S[26], C27, A[26], B[26], C26),
FA27(S[27], C28, A[27], B[27], C27),

FA25(S[25], C26, A[25], B[25], C25),
FA26(S[26], C27, A[26], B[26], C26),
FA27(S[27], C28, A[27], B[27], C27),

FA28(S[28], C29, A[28], B[28], C28),
FA29(S[29], C30, A[29], B[29], C29),
FA30(S[30], C31, A[30], B[30], C30),
FA31(S[31], C, A[31], B[31], C31);
endmodule

```

Full_adder is a different custom module that achieve full adder operation. Also it uses half_adder inside.

SUB operation:

SUB_test

[illegible]

First, does one's complement after that to reach two's complement, adds 1 to number. After these 2 operation it's a simple adding operation

```

module mySub (R,C,A,B,C0);
input [31:0] A,B;
input C0;
output C;
output [31:0] R;
wire [31:0] twosCompRes;
wire [31:0] onesCompRes;
//1's complement of B:
genvar i;
generate
    for(i = 0; i<32; i = i+1) begin: f1
        not n0(onesCompRes[i],B[i]);
    end
endgenerate
//B' + 1 twos Complement
Adder_32b g1(.A(onesCompRes), .B(32'b 000000000000000000000000000001), .S(twosCompRes), .C(C),.C0(C0));

//A+B
Adder_32b g2(.S(R), .A(A), .B(twosCompRes), .C(C),.C0(C0));
/*generate
    for(i = 0; i<32; i = i+1) begin: f2
        or or1(R[i],R[i],twosCompRes[i]);
    end
endgenerate*/
endmodule

```

AND operation:

AND_test.v

```

VSIM 11> run
# time = 0, A =000000000000000000001111111111110, B=111111111111110001110000000001, S=110, Result=00000000000000000001110000000000
VSIM 12> run
# time = 10, A =00111111111111000000000000000000, B=000001111111111111000111000001, S=110, Result=00000111111111110000000000000000

```

```

module myAnd( output [31:0] R, input [31:0] A, input [31:0] B);

genvar i;

generate
    for(i=0; i<32; i=i+1) begin: f1
        and g01(R[i], A[i], B[i]);
    end
endgenerate

```

And operation takes 32 bit numbers and performs bit-by-bit

OR_test.v

```
VSIM 5> run  
# time = 0, A=0000000000000000001111111111110, B=11111111111110001110000000001, S=111, Result=111111111111100011111111111  
VSIM 6> run  
# time = 10, A=00111111111110000000000000000, B=00000111111111111000111000001, S=111, Result=00111111111111111000111000001
```

```
module myOr( output [31:0] R, input [31:0] A, input [31:0] B);

    genvar i;

    generate
    for(i=0; i<32; i=i+1) begin: f1
        or g01(R[i], A[i], B[i]);
    end
    endgenerate
endmodule
```

NOR_test.v

[illegible]

```
module myNor( output [31:0] R, input [31:0] A, input [31:0] B);

genvar i;

generate
    for(i=0; i<32; i=i+1) begin: f1
        nor g01(R[i], A[i], B[i]);
    end
endgenerate
```

Slt_test.v

[illegible]

Xor operation:

Doesn't work hocam :[

[illegible]


```

1 module myxor [output [31:0] R, input [31:0] A, input [31:0] B];
2
3 /*
4  * genvar i;
5  *
6  * generate
7  *   for(i=0; i<32; i=i+1) begin: f1
8  *     xor g01(R[i], A[i], B[i]);
9  *   end
10  * endgenerate
11  */
12
13 //wire [31:0] wxor;
14
15 xor g0(R[31],A[31], B[31]);
16 xor g1(R[30],A[30], B[30]);
17 xor g2(R[29],A[29], B[29]);
18 xor g3(R[28],A[28], B[28]);
19 xor g4(R[27],A[27], B[27]);
20
21
22 xor g5(R[26],A[26], B[26]);
23 xor g6(R[25],A[25], B[25]);
24 xor g7(R[24],A[24], B[24]);
25 xor g8(R[23],A[23], B[23]);
26 xor g9(R[22],A[22], B[22]);
27
28
29 xor g10(R[21],A[21], B[21]);
30 xor g11(R[20],A[20], B[20]);
31 xor g12(R[19],A[19], B[19]);
32 xor g13(R[18],A[18], B[18]);
33 xor g14(R[17],A[17], B[17]);
34
35
36 xor g15(R[16],A[16], B[16]);
37 xor g16(R[15],A[15], B[15]);
38 xor g17(R[14],A[14], B[14]);
39
40 xor g18(R[13],A[13], B[13]);
41 xor g19(R[12],A[12], B[12]);
42
43
44 xor g20(R[11],A[11], B[11]);
45 xor g21(R[10],A[10], B[10]);
46 xor g22(R[9],A[9], B[9]);
47 xor g23(R[8],A[8], B[8]);
48 xor g24(R[7],A[7], B[7]);
49
50
51 xor g25(R[6],A[6], B[6]);
52 xor g26(R[5],A[5], B[5]);
53 xor g27(R[4],A[4], B[4]);
54 xor g28(R[3],A[3], B[3]);
55 xor g29(R[2],A[2], B[2]);
56
57
58 xor g30(R[1],A[1], B[1]);
59 xor g31(R[0],A[0], B[0]);
60

```

Multiplexer:

```
1 module mux3x8(output Fout, input S0, input S1, input S2, input A, input B, input C, input D, input E, input F, input G, input H);
2
3     wire wS0not;
4     wire wS1not;
5     wire wS2not;
6     wire wAnd0;
7     wire wAnd1;
8     wire wAnd2;
9     wire wAnd3;
10    wire wAnd4;
11    wire wAnd5;
12    wire wAnd6;
13    wire wAnd7;
14
15    not n0(wS0not, S0);
16    not n1(wS1not, S1);
17    not n2(wS2not, S2);
18
19    //  $AS_0'S_1'S_2' + BS_0'S_1'S_2 + CS_0'S_1S_2' + DS_0'S_1S_2 + ES_0S_1'S_2' + FS_0S_1'S_2 + GS_0S_1S_2' + HS_0S_1S_2$ 
20
21    and ga0(wAnd0,A,wS0not,wS1not,wS2not);
22    and ga1(wAnd1,B,wS0not,wS1not,S2);
23    and ga2(wAnd2,C,wS0not,S1,wS2not);
24    and ga3(wAnd3,D,wS0not,S1,S2);
25    and ga4(wAnd4,E,S0,wS1not,wS2not);
26    and ga5(wAnd5,F,S0,wS1not,S2);
27    and ga6(wAnd6,G,S0,S1,wS2not);
28    and ga7(wAnd7,H,S0,S1,S2);
29
30    or go1(Fout,wAnd0,wAnd1,wAnd2,wAnd3,wAnd4,wAnd5,wAnd6,wAnd7);
31
32
33
34 endmodule
```

 

$$= A s_0' s_1' s_2' + B s_0' s_1' s_2 + C s_0' s_1 s_2' + D s_0' s_1 s_2 + E s_0 s_1' s_2' + F s_0 s_1' s_2 + G s_0 s_1 s_2' + H s_0 s_1 s_2$$

> No simplification

This is the main program. First I fill the 32 bit wires and carry operation bit-by-bit inside a for loop

```
module main_module(output [31:0] R, input [2:0] S, input [31:0] A, input [31:0] B);

    wire [31:0] wAdd;
    wire [31:0] wXor;
    wire [31:0] wSub;
    wire [31:0] wMult;
    wire [31:0] wSlt;
    wire [31:0] wNor;
    wire [31:0] wAnd;
    wire [31:0] wOr;
    wire [31:0] wMux0;
    wire [31:0] wMux1;
    wire C;
    wire C0;

    Adder_32b g0(.S(wAdd), .A(A), .B(B), .C(C), .C0(C0)); // ADD niyetine 000
    myXor g1(wXor,A,B); // XOR 001
    mySub g2(wSub,C,A,B, 1'b 0); // SUB niyetine 010
    myAnd g3(wMult,A,B); // MULT niyetine 011
    mySlt g4(wSlt,A,B); //myslt // SLT niyetine 100
    myNor g5(wNor,A,B); // NOR 101
    myAnd g6(wAnd,A,B); // AND 110
    myOr g7(wOr,A,B); // OR 111

    genvar i;
    generate
    for(i=0; i<32; i=i+1) begin:f1
        mux3x8 m1(.Fout(R[i]), .S0(S[0]), .S1(S[1]), .S2(S[2]), .A(wAdd[i]), .B(wXor[i]), .C(wSub[i]), .D(wMult[i]),
            .E(wSlt[i]), .F(wNor[i]), .G(wAnd[i]), .H(wOr[i]));
    end
    endgenerate
```